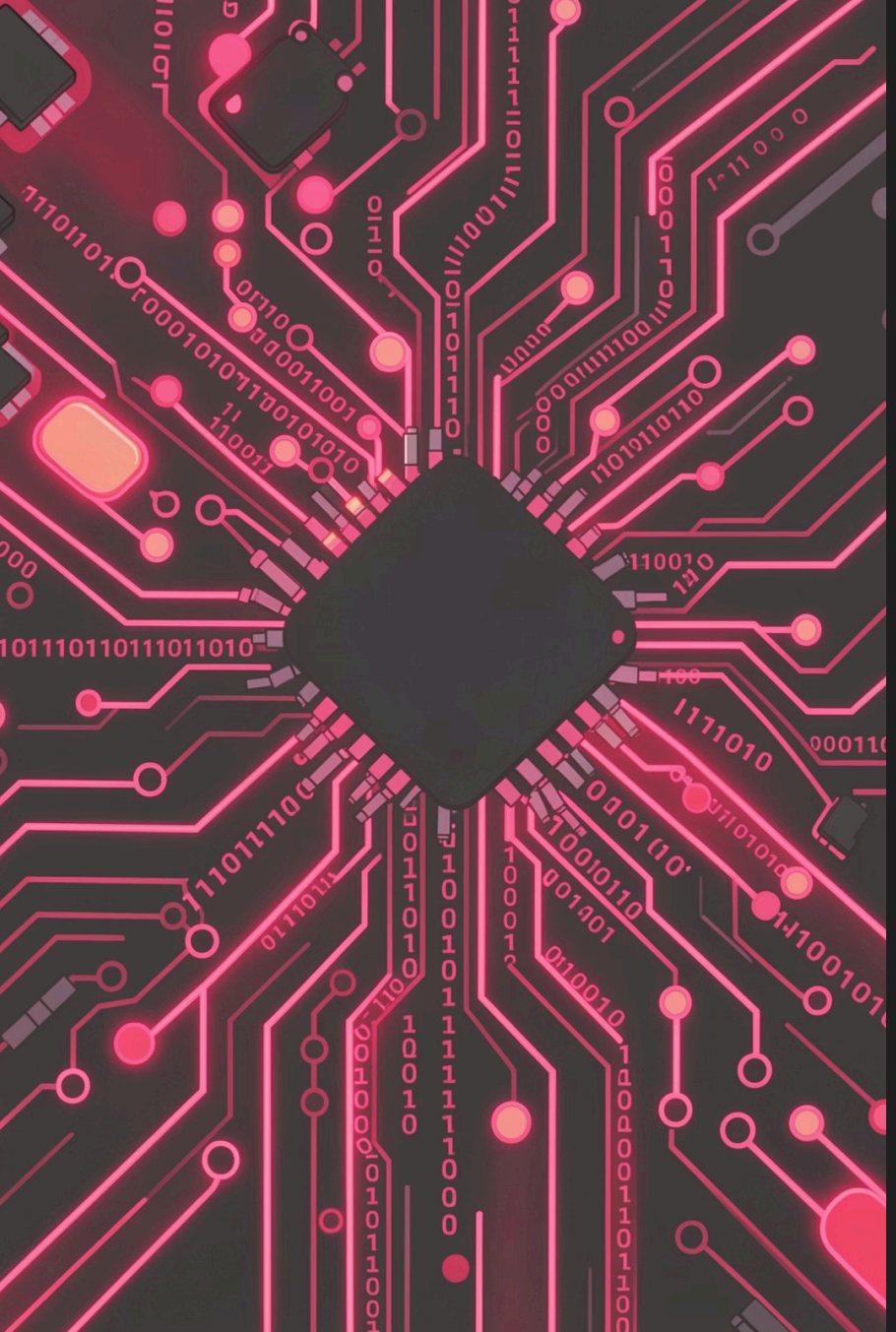

The Fundamentals of Digital Electronics

From binary signals to microchips — a guided tour through the logic that powers every modern device.

ENGINEERING ESSENTIALS

DIGITAL SYSTEMS

Made with GAMMA

Analog vs. Digital Signals

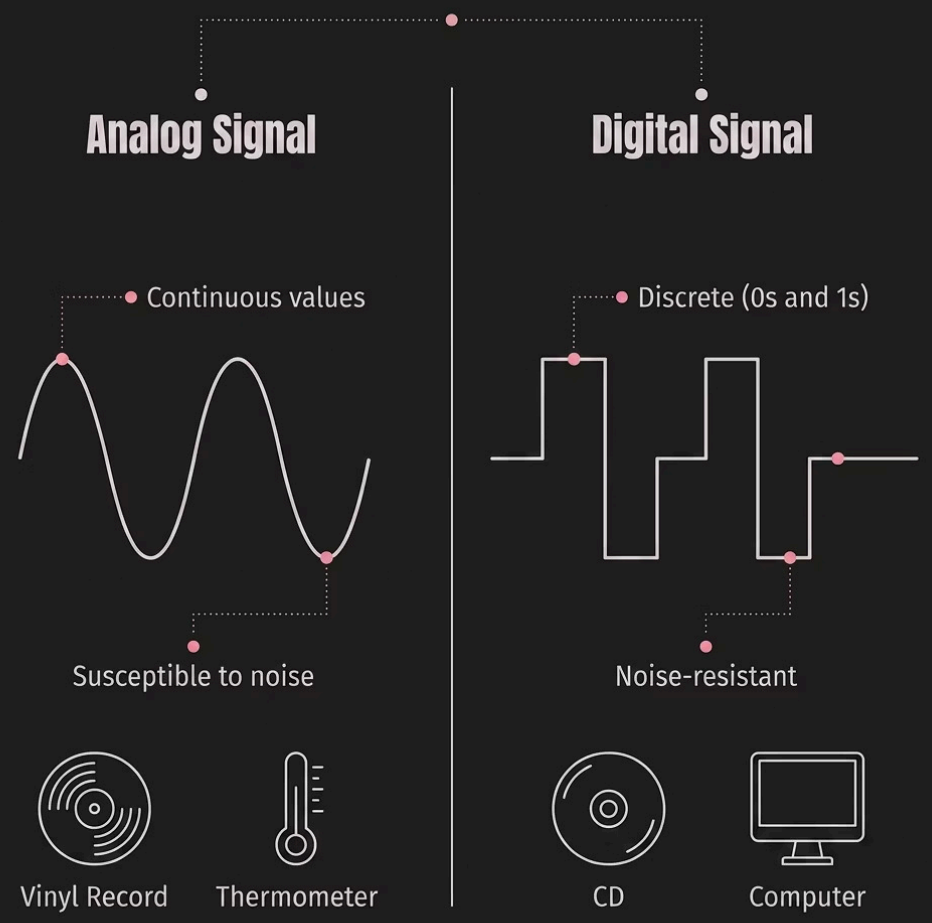

Why Digital Wins

Digital signals represent information as discrete **0s and 1s**, making them far more reliable than analog signals, which vary continuously and are prone to degradation.

- **Noise immunity** — small disturbances don't corrupt data
- **Easy to store and reproduce** without loss
- **Scalable** — from simple circuits to complex processors

Made with GAMMA

Binary Numbers: The Language of Computers

All digital systems communicate using **base-2 arithmetic** — only two symbols: 0 and 1.

Bit

The smallest unit — a single 0 or 1

Byte

8 bits together, representing one character

Decimal → Binary

5 in decimal = **101** in binary

Hexadecimal

Base-16 shorthand for binary, used in programming

Made with GAMMA

Logic Gates: The Building Blocks

Logic gates are physical circuits that perform **Boolean operations** on binary inputs to produce a single binary output.

AND Gate

Output is **1** only if *all* inputs are 1

OR Gate

Output is **1** if *any* input is 1

NOT Gate

Inverts the input: 0 → 1, 1 → 0

NAND / NOR

Universal gates — any logic function can be built from NAND alone

Made with GAMMA

Boolean Algebra: Designing with Logic

Developed by George Boole in 1854, **Boolean Algebra** provides the mathematical rules for manipulating logical expressions — the foundation of all digital circuit design.

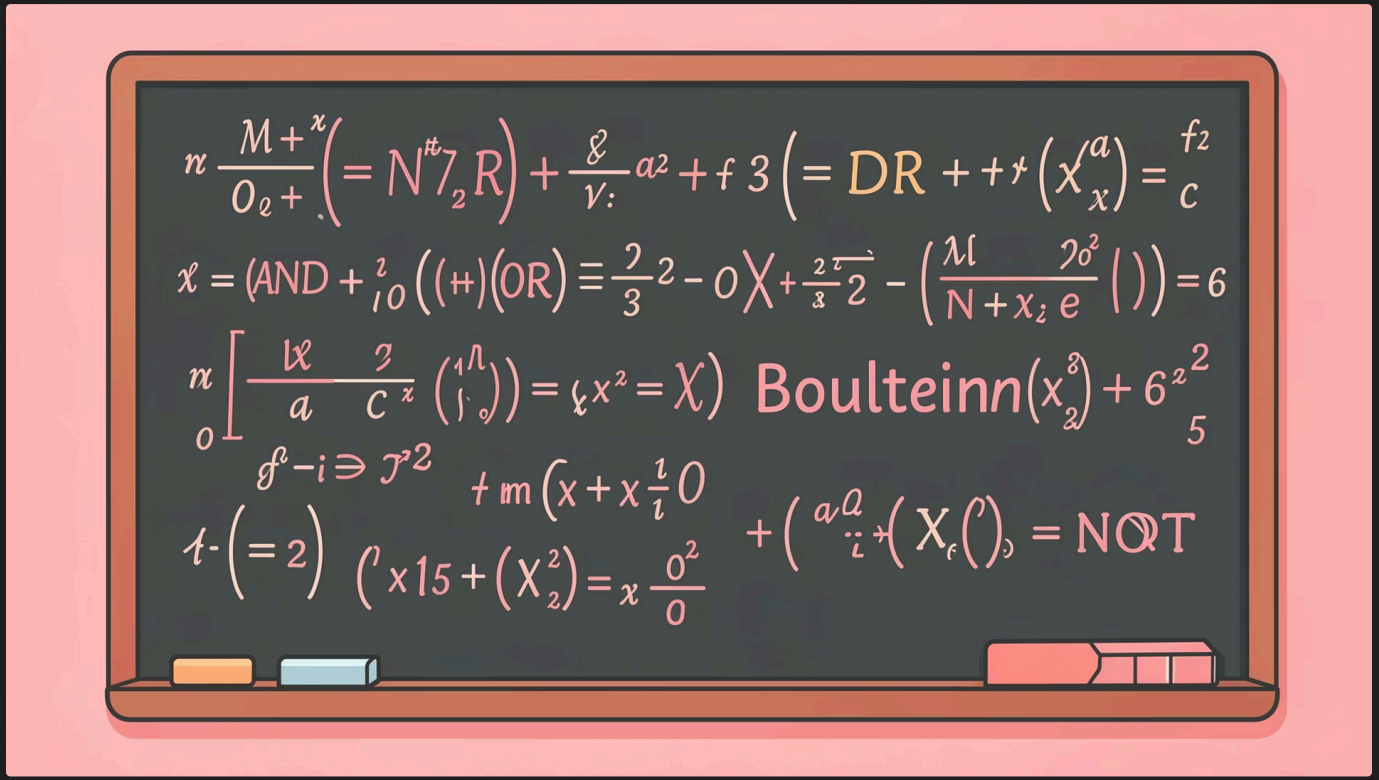

Commutative Law

A + B = B + A

Distributive Law

A · (B + C) = A·B + A·C

De Morgan's Theorem

¬(A·B) = ¬A + ¬B

Made with GAMMA

Combinational Logic: Making Decisions

In combinational circuits, **outputs depend only on current inputs** — no memory involved. The circuit reacts instantly.

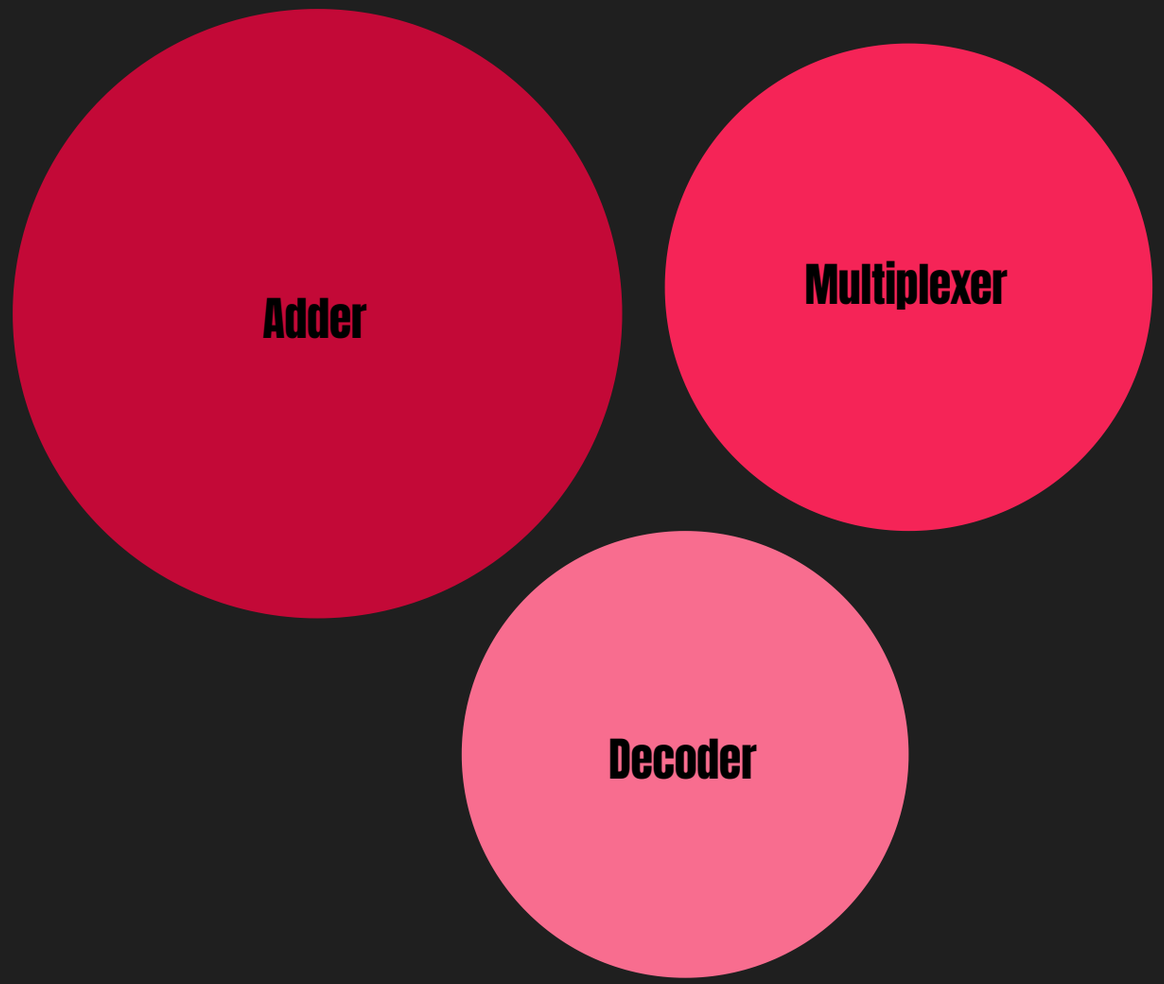

Common combinational circuits include adders, multiplexers, encoders, and decoders — each performing a specific logical function without storing any state.

Made with GAMMA

Sequential Logic: Remembering and Counting

Unlike combinational logic, **sequential circuits have memory** — their output depends on both current inputs *and* past states.

1

Flip-Flop

Stores 1 bit of data; the fundamental memory element

2

Register

A group of flip-flops storing multi-bit values

3

Counter

Sequentially counts clock pulses — used in timers and CPUs

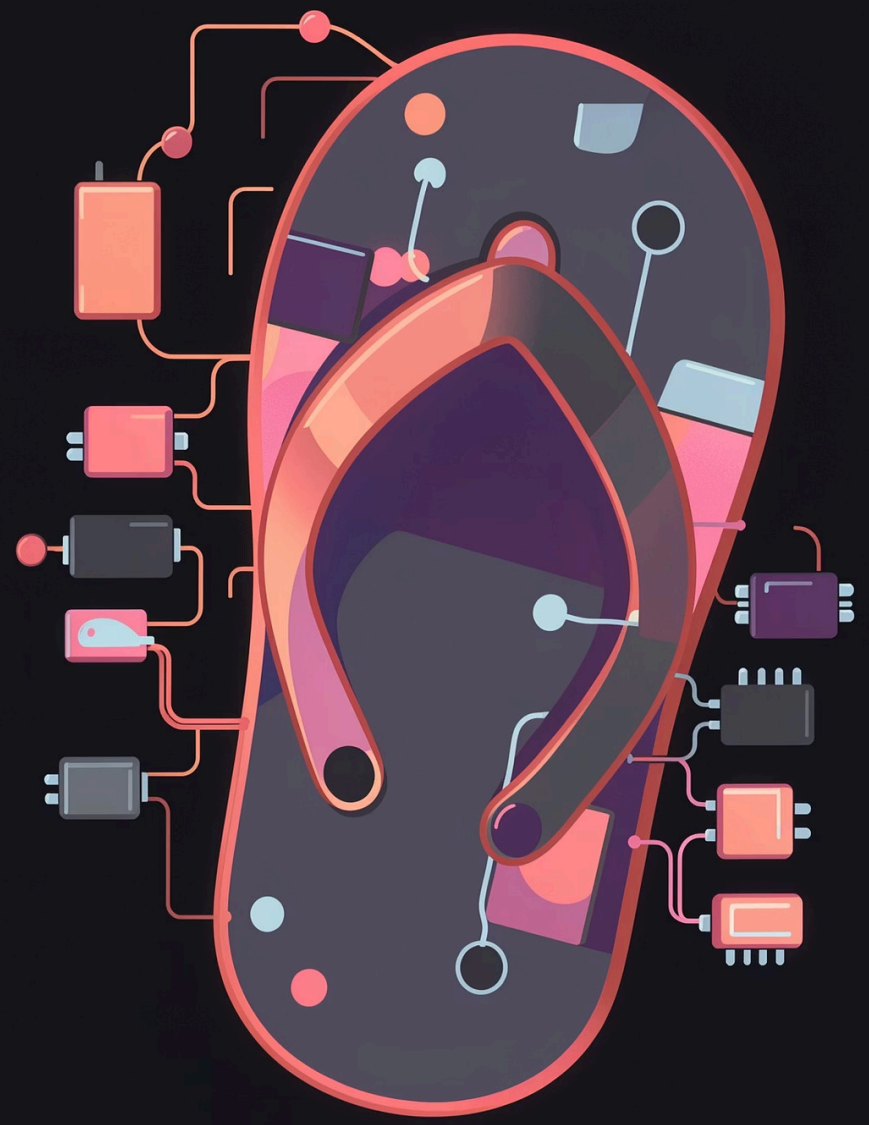

Made with GAMMA

Integrated Circuits: From Transistors to Chips

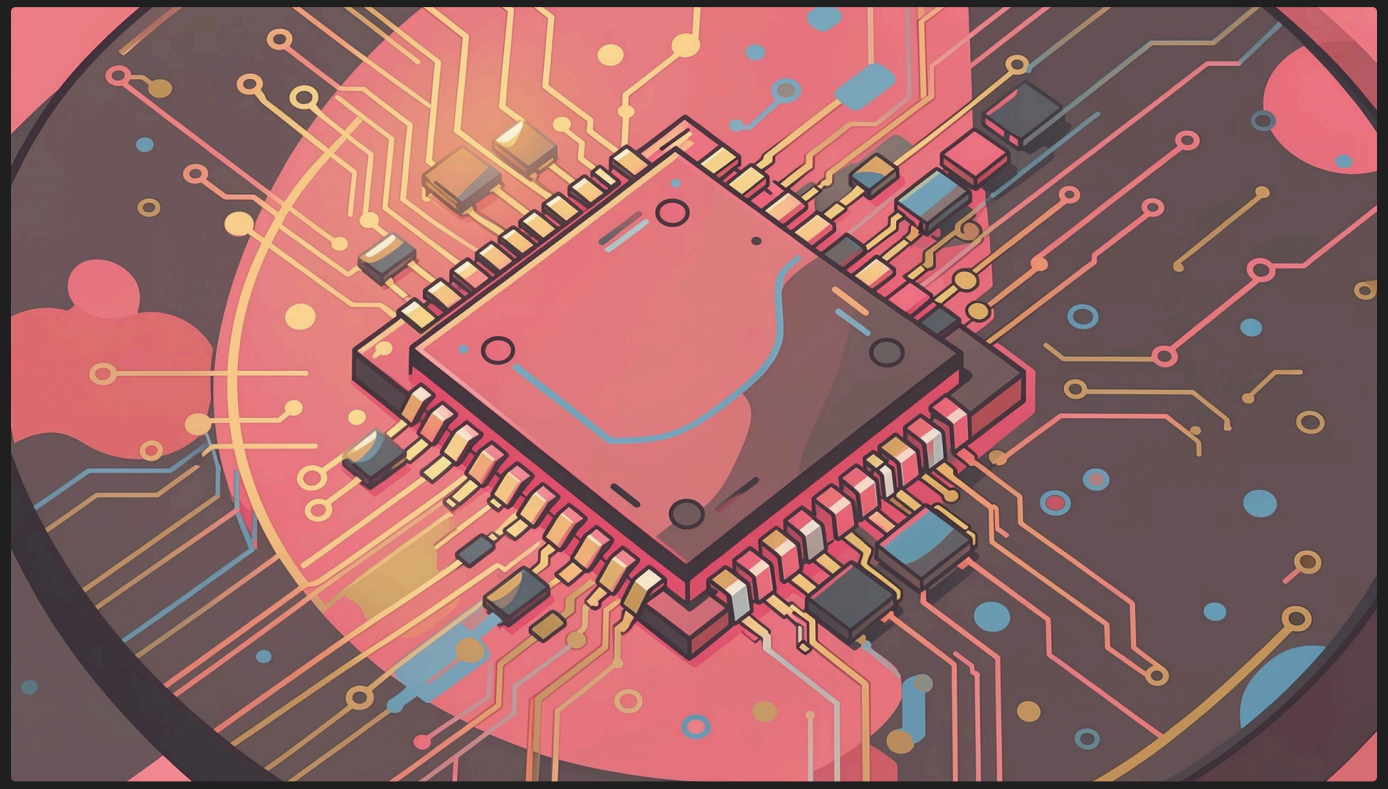

Moore's Law in Action

An integrated circuit packs **billions of transistors** onto a silicon wafer the size of a fingernail. Since 1965, transistor density has doubled roughly every two years.

SSI / MSI

Few to hundreds of gates

VLSI

Millions of transistors on one chip

Modern SoC

Entire systems on a single chip

Made with GAMMA

Digital Systems in the Real World

Digital electronics underpin **virtually every modern technology** — from your smartphone to medical devices and spacecraft.

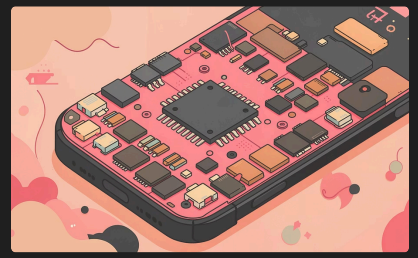

Consumer Electronics

Phones, laptops, and TVs rely on digital logic for processing and display

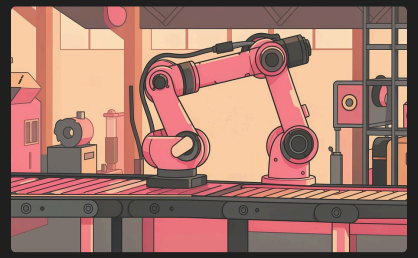

Industrial Automation

PLCs and microcontrollers drive robotics, manufacturing, and control systems

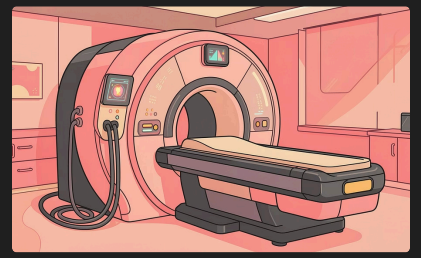

Medical Devices

Digital signal processing enables MRI, ECG, and diagnostic imaging

Made with GAMMA

Key Takeaways & Next Steps

01

Master the Basics

Binary math, logic gates, and Boolean algebra are your foundation

02

Build Circuits

Use simulators like Logisim or hardware like Arduino to experiment

03

Explore HDLs

Learn Verilog or VHDL to design and test digital systems programmatically

04

Go Deeper

Study computer architecture, microprocessors, and FPGA design

Remember: Every complex processor began as a simple AND gate. Start small, think logically, and build up.

Made with GAMMA